

## Using Microchip's Micropower LDOs

Author: Paul Paglia,  
Microchip Technology, Inc.

### INTRODUCTION

Microchip Technology, Inc.'s family of micropower LDOs utilizes low-voltage CMOS process technology. These LDOs provide similar ripple rejection and dropout characteristics as their bipolar equivalents, but are significantly more efficient. A typical bipolar regulator has base current equal to 1-2% of the output load, whereas Microchip's LDOs have approximately 60µA resulting in total operating current orders of magnitude lower than their bipolar counterparts. In addition, Microchip's LDOs can be placed in a shutdown mode, further enhancing their effectiveness in low-power applications.

This low-power operation makes Microchip's family of LDOs ideal for upgrading the LP2980 and MIC5205 bipolar LDOs in cellular phones, pagers, PDAs, laptops, hand-held meters, and other portable applications.

Microchip's micropower LDOs are available with fixed and adjustable outputs, supporting load currents up to 50mA, 100mA, 150mA and 300mA. SOT-23A-5, SOT-23A-6, SOT-223, and MSOP-8 packaging require minimal board space. Shutdown capability, thermal protection, and current limiting are standard in every device. Adjustable output, error flag, and noise bypass capability are provided on select devices (see Table 3).

### APPLICATIONS

#### Optimizing Output Voltage Accuracy of 1070/1071 Adjustable LDOs

Microchip's LDOs are available in both adjustable and fixed output voltage options. The accuracy of the output depends on the initial accuracy, stability, and temperature coefficient of the internal bandgap reference and the feedback resistors.

Rather than specifying  $V_{OUT}$  accuracy on adjustable regulators, the initial accuracy and temperature coefficient of the internal reference is specified.  $V_{OUT}$  accuracy is not specified because it depends on the external feedback resistors. Figure 1 shows a typical adjustable LDO feedback circuit in which resistors R1 and R2 set the output voltage per the following formula:

$$V_{OUT} = V_{REF} [(R1/R2) + 1]$$

Where:  $V_{REF} = 1.20V$

#### EQUATION 1:

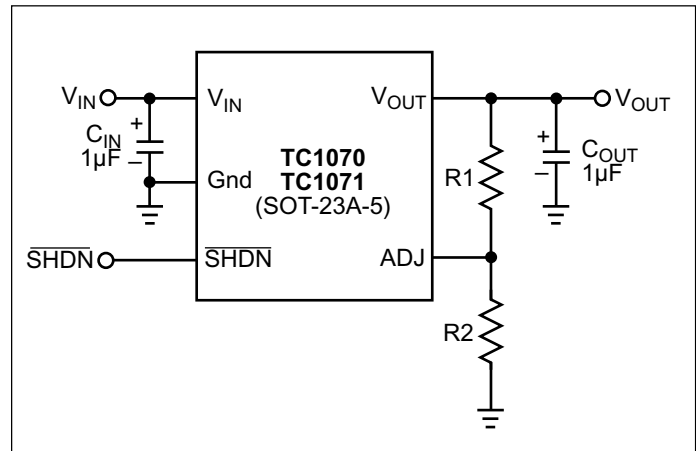


FIGURE 1: Adjustable LDO feedback circuit.

The ADJ pin is a high impedance CMOS input. Consequently, resistor values can be between 300KΩ and 1MΩ to minimize the current through R1 and R2.

Inspection of Equation 1 reveals the following:

1. When  $V_{OUT}$  is made equal to  $V_{REF}$  (i.e., R1 is zero), the tolerance of  $V_{OUT}$  will be approximately that of  $V_{REF}$ .
2. The tolerance of  $V_{OUT}$  is a function of both the tolerance of  $V_{REF}$  and the tolerance of the R1/R2 ratio when  $V_{OUT}$  is greater than  $V_{REF}$  (i.e., when  $R1/R2 > 0$ ).

For the purposes of worst case analysis, the tolerances of R1 and R2 are additive. For example, if R1 and R2 are both 1% resistors, the maximum tolerance of the R1/R2 ratio is 2%.

Re-examining the effect of tolerances on Equation 1 reveals that the tolerance of  $V_{OUT}$  worsens proportionally as the  $V_{OUT}$  setting departs the value of  $V_{REF}$ . Stated another way:

$$ERROR_{V_{OUT}} \propto (V_{OUT} - V_{REF})$$

#### EQUATION 2:

Table 1 shows that percentage of total output voltage error contributed by the tolerances of  $V_{REF}$  and R1/R2 for various values of  $V_{OUT}$ .

# AN41

V <sub>OUT</sub> (V)	Reference Tolerance (%)	Resistor Tolerance (%)	Resistor Error (%)	Total Output Error (%)
1.23	2	1	0	2
1.23	2	2	0	2
2.0	2	1	0.77	2.77
2.0	2	2	1.54	3.54
2.46	2	1	1.0	3.0
2.46	2	2	2.0	4.0
3.0	2	1	1.2	3.2
3.0	2	2	2.4	4.2
4.0	2	1	1.38	3.38
4.0	2	2	2.76	4.76
5.0	2	1	1.50	3.5
5.0	2	2	3.0	5.0

**TABLE 1:** Output error contributors.

The output voltage accuracy of the adjustable regulator improves with tighter tolerance resistors. However, accuracy will be limited to  $\pm 2\%$  due to the accuracy of the reference. Table 2 shows output voltage accuracy for the adjustable LDO using 1%, 0.5%, and 0.1% tolerance resistors.

V <sub>OUT</sub>	V <sub>OUT</sub> Error		
	1% Resistor Tol.	0.5% Resistor Tol.	0.1% Resistor Tol.
5.0V	3.5%	2.75%	2.15%
4.0V	3.38%	2.69%	2.14%
3.0V	3.2%	2.6%	2.12%
2.46V	3.0%	2.5%	2.10%
2.0V	2.77%	2.39%	2.08%
1.23V	2.0%	2.0%	2.0%

**TABLE 2:** Resistor tolerance effect on V<sub>OUT</sub> error.

## Power-Saving Shutdown Mode

All of Microchip's micropower LDOs have a shutdown input that allows the user to digitally disconnect the load from the power source and send the regulator into a low-power "sleep" mode. The supply current is reduced from 50 $\mu$ A, during normal operation, to 0.05 $\mu$ A in shutdown.

The  $\overline{\text{SHDN}}$  pin input current is guaranteed to be no greater than 1 $\mu$ A (an order of magnitude lower than bipolar counterparts).

Shutdown mode is activated when  $\overline{\text{SHDN}}$  is below  $0.2 \times V_{\text{IN}}$ . In this mode, the pass transistor is turned OFF, disconnecting the load from the power source.


Shutdown mode is disabled, allowing normal device operation, when the input is above  $0.4 \times V_{\text{IN}}$ . This V<sub>IN</sub> is low enough to ensure that a control output from a 3.3V microcontroller, operating from four fully-charged NiCad/NiMH cells (6V), can enable the LDO. If not used,  $\overline{\text{SHDN}}$  should not be left floating, but rather connected to V<sub>IN</sub>.

## Out-of-Regulation ( $\overline{\text{ERROR}}$ ) Flag

The TC1070/1/2/3 and TC1054/5 each have Error Flag outputs that are asserted when the LDO falls out of regulation by approximately  $-5\%$ .


The  $\overline{\text{ERROR}}$  pin is an N-channel open drain output that can sink up to 1mA. However, larger value pull-up resistors should be selected so that energy loss through  $\overline{\text{ERROR}}$  is kept to a minimum.  $\overline{\text{ERROR}}$  must be pulled to any supply voltage less than 7V through a pull-up resistor.

$\overline{\text{ERROR}}$  output is valid for input voltages above 1V and undefined for voltages below 1V. As the output is transitioning between 0V and 1.0V during power up/down, the Error output may float momentarily to 1.0V. If 1.0V is high enough to be interpreted as a logic 1, the two-resistor network shown in Figure 3 may be used. This will ensure that  $\overline{\text{ERROR}}$  never will rise above 0.5V during invalid states. Keep in mind the maximum that Error output can be in its high state is V<sub>OUT</sub>/2.

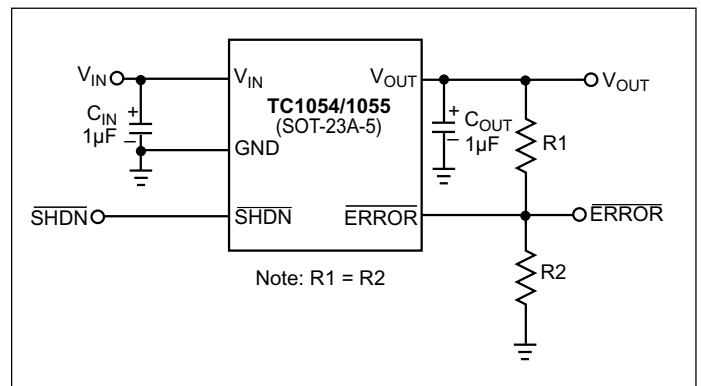

**FIGURE 2:** Ensuring valid error output for low V<sub>IN</sub> levels.

By connecting an RC on  $\overline{\text{ERROR}}$  output, it can be used as a power on reset. During power up, the Error comparator will go high as soon as the regulator output is within tolerance.  $\overline{\text{ERROR}}$  will be delayed by the RC network before releasing the microcontroller from reset.

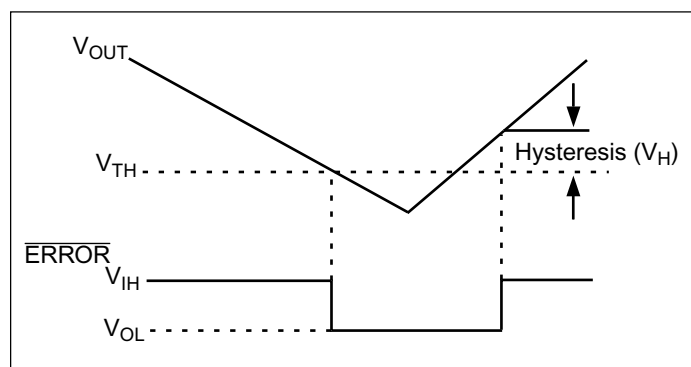

**FIGURE 3:** Out-of-regulation error flag.

$\overline{\text{ERROR}}$  also can be used as a power quality monitor. If a low input voltage or an over-current condition causes the output to fall out of regulation,  $\overline{\text{ERROR}}$  will pull low, signifying an unstable power condition. This flags the microcontroller, which now can activate proper shutdown sequencing, ensuring orderly system operation.

The Error comparator has 50mV of positive hysteresis to provide some  $V_{IN}$  noise immunity.

### Input, Output and Bypass Capacitors

It is recommended that input, output, and bypass capacitors be used for optimal device performance. To ensure stability in the LDO's feedback loop, a capacitor is required from the output to ground (Figures 4 and 5). Capacitors must be chosen that meet the ESR value range and minimum capacitance identified in device datasheets. In general, a 1 $\mu$ F-2.2 $\mu$ F capacitor is recommended to ensure stable operation under maximum load conditions. Larger value capacitors (4.7 to 10 $\mu$ F) will increase transient load response and ripple rejection performance.

Ceramic capacitors offer the lowest ESR followed by, in order of increasing ESR, OS-CON, film, aluminum electrolytic, and tantalum. Film capacitors provide good performance, but usually are not a viable solution due to excessive cost and size. Ceramics combine excellent ESR with relatively small size. However, the ESR of ceramic capacitors sometimes can be too low, requiring a 1 $\Omega$  series resistor to ensure stability. OS-CON capacitors offer an ESR only slightly higher than ceramics, but consume more volume. The OS-CON capacitors exhibit rock-solid ESR from -55 $^{\circ}$ C to 125 $^{\circ}$ C. Aluminum electrolytics are ideal for low-cost commercial temperature grade applications where board space is not a concern. Like OS-CON capacitors, electrolytics typically are offered in a radial lead package, but are available in surface mount styles. Tantalums

offer an ESR similar to aluminum electrolytics. They also provide a reasonable cost, high-volume efficiency solution and are usually the capacitor of choice.

A 1 $\mu$ F input capacitor should be installed from  $V_{CC}$  to GND (Figures 4 and 5) if the IC is powered from a battery or if there is excessive (>1ft) distance between the regulator and the AC filter capacitor. A larger value capacitor will provide better  $V_{CC}$  noise rejection and improved performance when the supply has a high AC impedance. A 470pf bypass capacitor can be tied to the bypass pin on the TC1014/1015 and TC1072/1073 or the ADJ pin on the TC1070/1071 (see Figure 5) to reduce the  $V_{REF}$  noise.

### Thermal Issues

The amount of power that the LDO dissipates is a function of the bias supply current and the pass-through current. The pass-through current is the current that flows from  $V_{CC}$  through the pass transistor of the LDO to the load. The following equation is used to calculate power dissipation:

$$P_D = (V_{CC} \times I_S) + [(V_{CC} - V_{OUT}) I_{LOAD}]$$

#### EQUATION 3:

Maximum values of  $V_{CC}$  and  $I_{LOAD}$  and minimum values for  $V_{OUT}$  should be used when calculating  $P_D$  to ensure worst case conditions are met.

The amount of power that the LDO can dissipate depends on the ambient temperature ( $T_A$ ). A guardbanded maximum die temperature ( $T_{JMAX}$ ) of 125 $^{\circ}$ C is used to account for variations in thermal conductivity of PC boards and variations in airflow.

$$\theta_{JA} = (T_{JMAX} - T_A) / P_{DMAX}$$

$$\theta_{JA} = \theta_{JC} + \theta_{CA}$$

#### EQUATION 4:

$\theta_{JC}$  is the thermal resistance from the die surface to the package body and leads.  $\theta_{CA}$  is the thermal resistance from the package body and leads to the surrounding air, PC board dielectric, and traces.

The SOT-23A-5 and SOT-23A-6 packages have a worst case  $\theta_{JA}$  of 220 $^{\circ}$ C/W when mounted on a single-layer FR4 dielectric copper-clad PC board. This  $\theta_{JA}$  can be reduced by using a PC board made with a dielectric that has a better heat transfer coefficient. Additionally, adding a ground plane and large supply traces to the IC will provide better thermal conductivity. The values for  $\theta_{JA}$  are for a system that uses natural convection. A significant reduction in  $\theta_{CA}$  can be induced with forced airflow.

$$\text{Given: } \theta_{JA} = 220^{\circ}\text{C/W}$$

$$\therefore P_{DMAX} = (125^{\circ}\text{C} - T_A) / 220^{\circ}\text{C/W}$$

# AN41

Ambient Temperature	$P_{DMAX}$
25°C	0.454W
50°C	0.341W
85°C	0.182W

Excessive power dissipation will result in elevated die temperatures that could activate the device's thermal shutdown. The LDOs have an integrated thermal protection circuitry that disables the LDO when die temperatures exceed approximately 160°C. Ten degrees Celsius of hysteresis is built into the protection circuitry, such that the LDO is not released from thermal shutdown until the die temperature drops to 150°C. In addition to thermal protection, an internal sense resistor in series with the pass element provides a short-circuit limit.

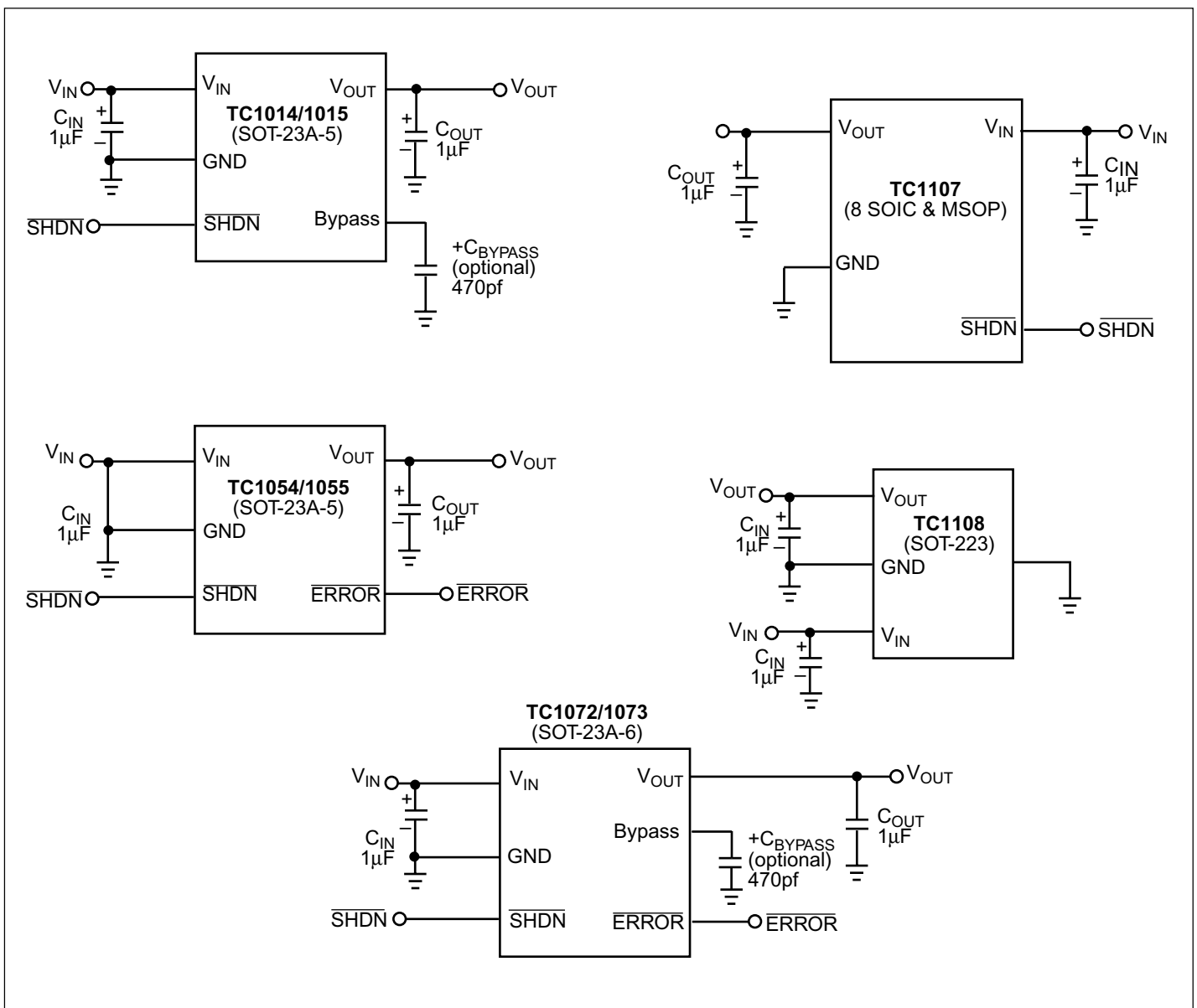


FIGURE 4: Typical application circuit (fixed output).

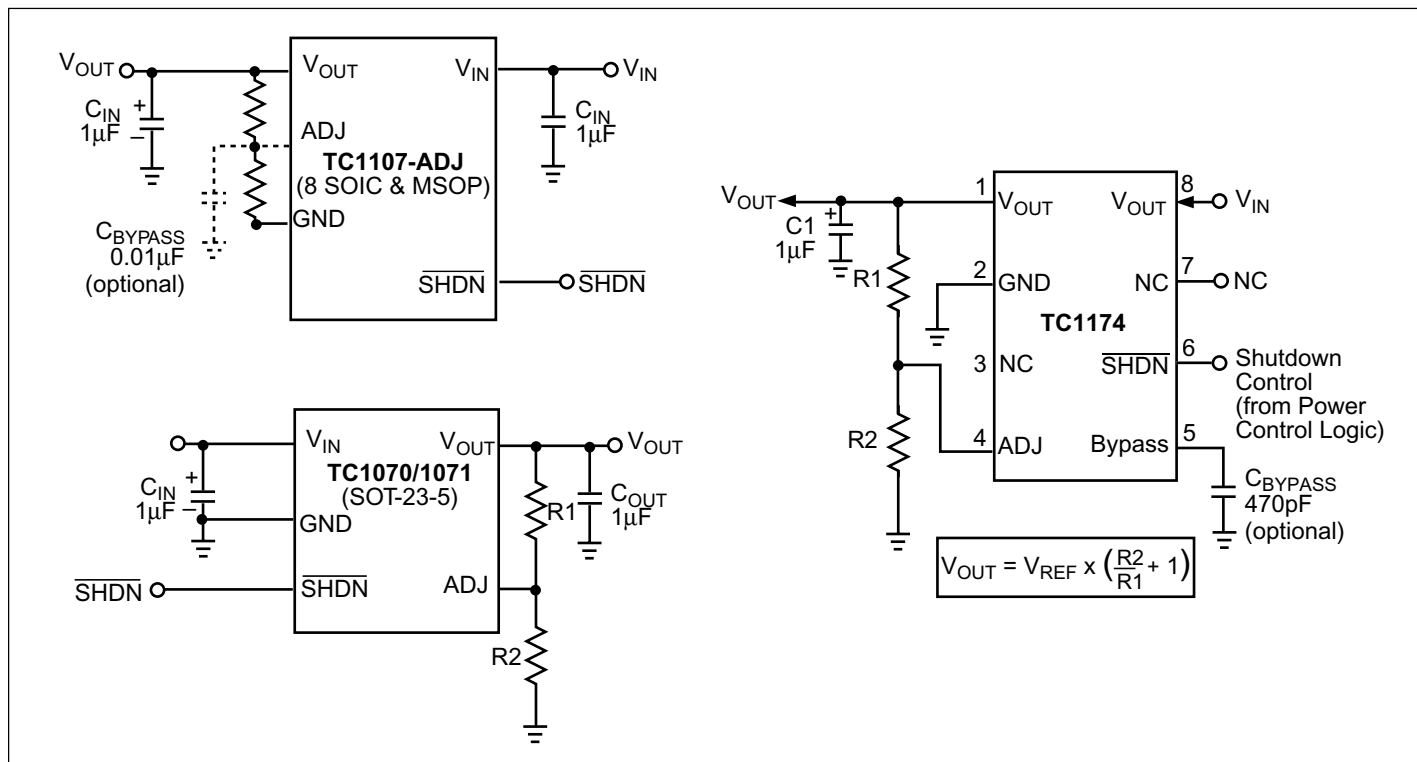


FIGURE 5: Typical application circuit (adjustable output).

Part No.	Package	Output Voltage**											Adj	SHDN	Error Flag	Bypass	I <sub>SS</sub> Typ. (µA)	I <sub>OUT</sub> Max (mA)	V <sub>DROP</sub> Typ. (mV)	
		2.5V	2.7V	2.8V	2.84V	2.85V	3.0V	3.15V	3.3V	3.6V	4.0V	5.0V								
TC1014	SOT-23A-5	X	X			X	X			X	X	X	X		X		X	50	50	85
TC1015	SOT-23A-5	X	X			X	X			X	X	X	X		X		X	50	100	180
TC1054	SOT-23A-5	X	X			X	X			X	X	X	X		X	X		50	50	85
TC1055	SOT-23A-5	X	X			X	X			X	X		X		X	X		50	100	180
TC1070	SOT-23A-5													X	X			50	50	85
TC1071	SOT-23A-5													X	X			50	100	180
TC1072	SOT-23A-6	X	X			X	X			X	X	X	X		X		X	50	50	85
TC1073	SOT-23A-6	X	X			X	X			X	X	X	X		X		X	50	100	180
TC1107	MSOP-8, SO-8			X			X			X			X		X		X	50	300	240
TC1108	SOT-223			X			X			X			X					50	300	240
TC1173	MSOP-8, SO-8			X			X			X			X		X	X	X	50	100	180
TC1174	MSOP-8, SO-8													X	X		X	50	300	240
TC1185	SOT-23A-5	X	X			X	X			X	X	X	X		X		X	50	150	270
TC1186	SOT-23A-5	X	X			X	X			X	X	X	X		X	X		50	150	270
TC1187	SOT-23A-5													X	X	X		50	150	270
TC1188*	SOT-23A-5			X	X					X					X			50	100	55
TC1189*	SOT-23A-5			X	X					X					X			50	100	55
TC1223	SOT-23A-5	X	X			X	X			X	X	X	X		X			50	50	85
TC1224	SOT-23A-5	X	X			X	X			X	X	X	X		X			50	100	180

Notes: \*Pin Compatible Replacement for MAX8863/8864

\*\*Custom Output Voltages Available – Contact Microchip Technology

TABLE 3: CMOS LDOs selection guide.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

## Trademarks


The Microchip name and logo, the Microchip logo, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, KEELOQ, SEEVAL, MPLAB and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


Total Endurance, ICSP, In-Circuit Serial Programming, Filter-Lab, MXDEV, microID, *FlexROM*, *fuzzyLAB*, MPASM, MPLINK, MPLIB, PICC, PICDEM, PICDEM.net, ICEPIC, Migratable Memory, FanSense, ECONOMONITOR, Select Mode and microPort are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Term Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2001, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

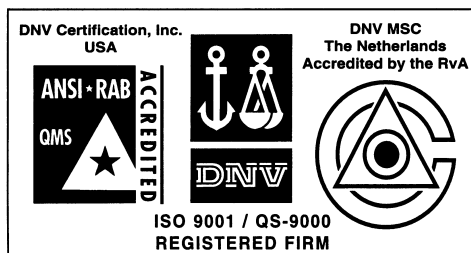

*Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.*



# MICROCHIP

## WORLDWIDE SALES AND SERVICE

### AMERICAS

#### Corporate Office

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7200 Fax: 480-792-7277  
Technical Support: 480-792-7627  
Web Address: <http://www.microchip.com>

#### Rocky Mountain

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7966 Fax: 480-792-7456

#### Atlanta

500 Sugar Mill Road, Suite 200B  
Atlanta, GA 30350  
Tel: 770-640-0034 Fax: 770-640-0307

#### Austin - Analog

13740 North Highway 183  
Building J, Suite 4  
Austin, TX 78750  
Tel: 512-257-3370 Fax: 512-257-8526

#### Boston

2 Lan Drive, Suite 120  
Westford, MA 01886  
Tel: 978-692-3848 Fax: 978-692-3821

#### Boston - Analog

Unit A-8-1 Millbrook Tarry Condominium  
97 Lowell Road  
Concord, MA 01742  
Tel: 978-371-6400 Fax: 978-371-0050

#### Chicago

333 Pierce Road, Suite 180  
Itasca, IL 60143  
Tel: 630-285-0071 Fax: 630-285-0075

#### Dallas

4570 Westgrove Drive, Suite 160  
Addison, TX 75001  
Tel: 972-818-7423 Fax: 972-818-2924

#### Dayton

Two Prestige Place, Suite 130  
Miamisburg, OH 45342  
Tel: 937-291-1654 Fax: 937-291-9175

#### Detroit

Tri-Atria Office Building  
32255 Northwestern Highway, Suite 190  
Farmington Hills, MI 48334  
Tel: 248-538-2250 Fax: 248-538-2260

#### Los Angeles

18201 Von Karman, Suite 1090  
Irvine, CA 92612  
Tel: 949-263-1888 Fax: 949-263-1338

#### New York

150 Motor Parkway, Suite 202  
Hauppauge, NY 11788  
Tel: 631-273-5305 Fax: 631-273-5335

#### San Jose

Microchip Technology Inc.  
2107 North First Street, Suite 590  
San Jose, CA 95131  
Tel: 408-436-7950 Fax: 408-436-7955

#### Toronto

6285 Northam Drive, Suite 108  
Mississauga, Ontario L4V 1X5, Canada  
Tel: 905-673-0699 Fax: 905-673-6509

### ASIA/PACIFIC

#### Australia

Microchip Technology Australia Pty Ltd  
Suite 22, 41 Rawson Street  
Epping 2121, NSW  
Australia  
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

#### China - Beijing

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Beijing Liaison Office  
Unit 915  
Bei Hai Wan Tai Bldg.  
No. 6 Chaoyangmen Beidajie  
Beijing, 100027, No. China  
Tel: 86-10-85282100 Fax: 86-10-85282104

#### China - Chengdu

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Chengdu Liaison Office  
Rm. 2401, 24th Floor,  
Ming Xing Financial Tower  
No. 88 TIDU Street  
Chengdu 610016, China  
Tel: 86-28-6766200 Fax: 86-28-6766599

#### China - Fuzhou

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Fuzhou Liaison Office  
Rm. 531, North Building  
Fujian Foreign Trade Center Hotel  
73 Wusi Road  
Fuzhou 350001, China  
Tel: 86-591-7557563 Fax: 86-591-7557572

#### China - Shanghai

Microchip Technology Consulting (Shanghai)  
Co., Ltd.  
Room 701, Bldg. B  
Far East International Plaza  
No. 317 Xian Xia Road  
Shanghai, 200051  
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

#### China - Shenzhen

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Shenzhen Liaison Office  
Rm. 1315, 13/F, Shenzhen Kerry Centre,  
Renminnan Lu  
Shenzhen 518001, China  
Tel: 86-755-2350361 Fax: 86-755-2366086

#### Hong Kong

Microchip Technology Hongkong Ltd.  
Unit 901-6, Tower 2, Metroplaza  
223 Hing Fong Road  
Kwai Fong, N.T., Hong Kong  
Tel: 852-2401-1200 Fax: 852-2401-3431

#### India

Microchip Technology Inc.  
India Liaison Office  
Divyasree Chambers  
1 Floor, Wing A (A3/A4)  
No. 11, O'Shaughnessey Road  
Bangalore, 560 025, India  
Tel: 91-80-2290061 Fax: 91-80-2290062

### Japan

Microchip Technology Japan K.K.  
Benex S-1 6F  
3-18-20, Shinyokohama  
Kohoku-Ku, Yokohama-shi  
Kanagawa, 222-0033, Japan  
Tel: 81-45-471-6166 Fax: 81-45-471-6122

### Korea

Microchip Technology Korea  
168-1, Youngbo Bldg. 3 Floor  
Samsung-Dong, Kangnam-Ku  
Seoul, Korea 135-882  
Tel: 82-2-554-7200 Fax: 82-2-558-5934

### Singapore

Microchip Technology Singapore Pte Ltd.  
200 Middle Road  
#07-02 Prime Centre  
Singapore, 188980  
Tel: 65-334-8870 Fax: 65-334-8850

### Taiwan

Microchip Technology Taiwan  
11F-3, No. 207  
Tung Hua North Road  
Taipei, 105, Taiwan  
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

### EUROPE

#### Denmark

Microchip Technology Denmark ApS  
Regus Business Centre  
Lautrup høj 1-3  
Ballerup DK-2750 Denmark  
Tel: 45 4420 9895 Fax: 45 4420 9910

#### France

Arizona Microchip Technology SARL  
Parc d'Activite du Moulin de Massy  
43 Rue du Saule Trapu  
Batiment A - 1er Etage  
91300 Massy, France  
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

#### Germany

Arizona Microchip Technology GmbH  
Gustav-Heinemann Ring 125  
D-81739 Munich, Germany  
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

#### Germany - Analog

Lochamer Strasse 13  
D-82152 Martinsried, Germany  
Tel: 49-89-895650-0 Fax: 49-89-895650-22

#### Italy

Arizona Microchip Technology SRL  
Centro Direzionale Colleoni  
Palazzo Taurus 1 V. Le Colleoni 1  
20041 Agrate Brianza  
Milan, Italy  
Tel: 39-039-65791-1 Fax: 39-039-6899883

#### United Kingdom

Arizona Microchip Technology Ltd.  
505 Eskdale Road  
Winnersh Triangle  
Wokingham  
Berkshire, England RG41 5TU  
Tel: 44 118 921 5869 Fax: 44-118 921-5820

08/01/01