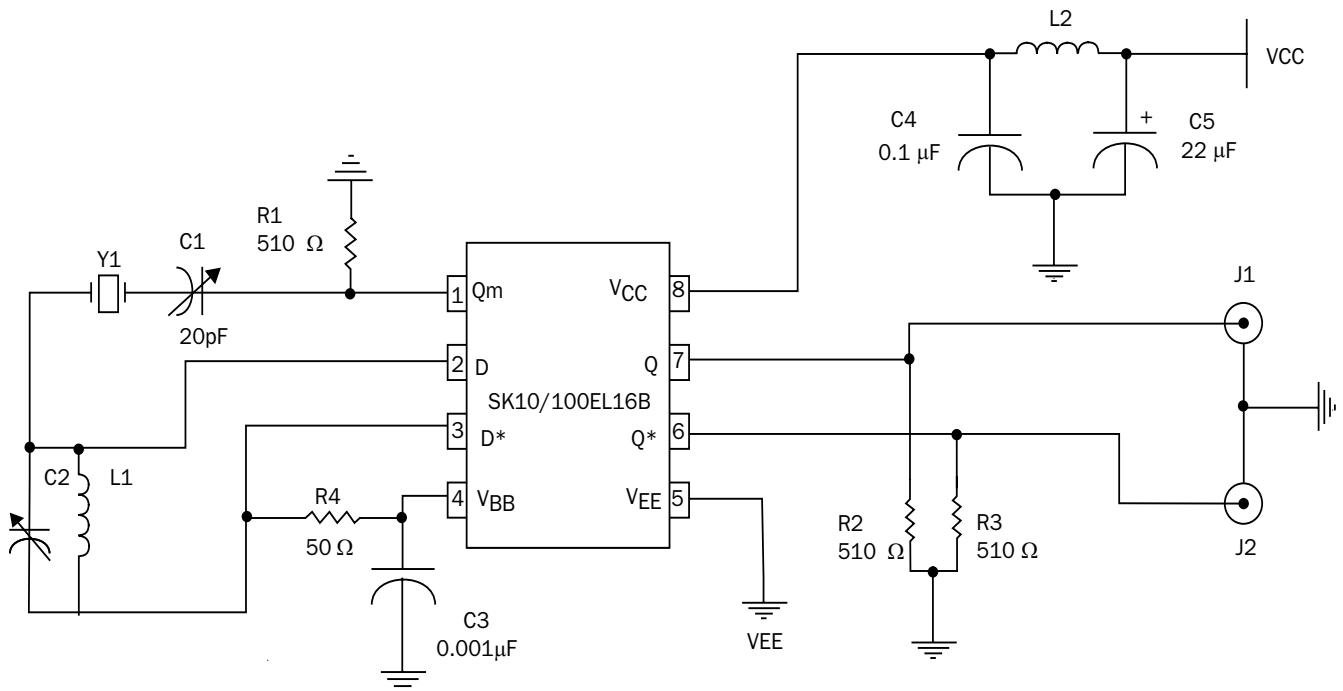


HIGH-PERFORMANCE PRODUCTS
Voltage Controlled and Overtone Crystal Oscillators

Crystal oscillators are used to provide reference frequency clocks for applications such as SONET, Gigabit Ethernet, or fiber channel. Crystal oscillator manufacturers can design oscillators with accurate signal waveforms of ± 10 ppm or better of the reference frequency. In this application note only examples of overtone and voltage controlled crystal oscillators are provided in figures 1, 2, 3, and 4, respectively.

These reference clocks can also be obtained with a PLL based IC devices. Some of the most popular reference frequencies are 155.52 MHz (OC-3) and 622.08 MHz (OC-12) which can be obtained using Semtech's PLL based devices mentioned in Table 1.

Device	Function	Package Type	Operating Voltage
SK1801W	SONET OC - 3 Frequency Synthesizer	16 Pin Wide Body SOIC	3.0V to 5.5V
SK1802W	SONET OC - 12 Frequency Synthesizer	16 Pin Wide Body SOIC	3.0V to 5.5V

Table 1

Figure 1: Overtone Crystal Oscillator

HIGH-PERFORMANCE PRODUCTS
Overtone Crystal Oscillators

Overtone operation is accomplished by adjusting the tank circuit frequency at or near the desired frequency. Using formula 1, we can calculate the values of L1 and C1 for a desired frequency.

$$f \cong \frac{1}{2 \pi \sqrt{L_1 C_1}}$$

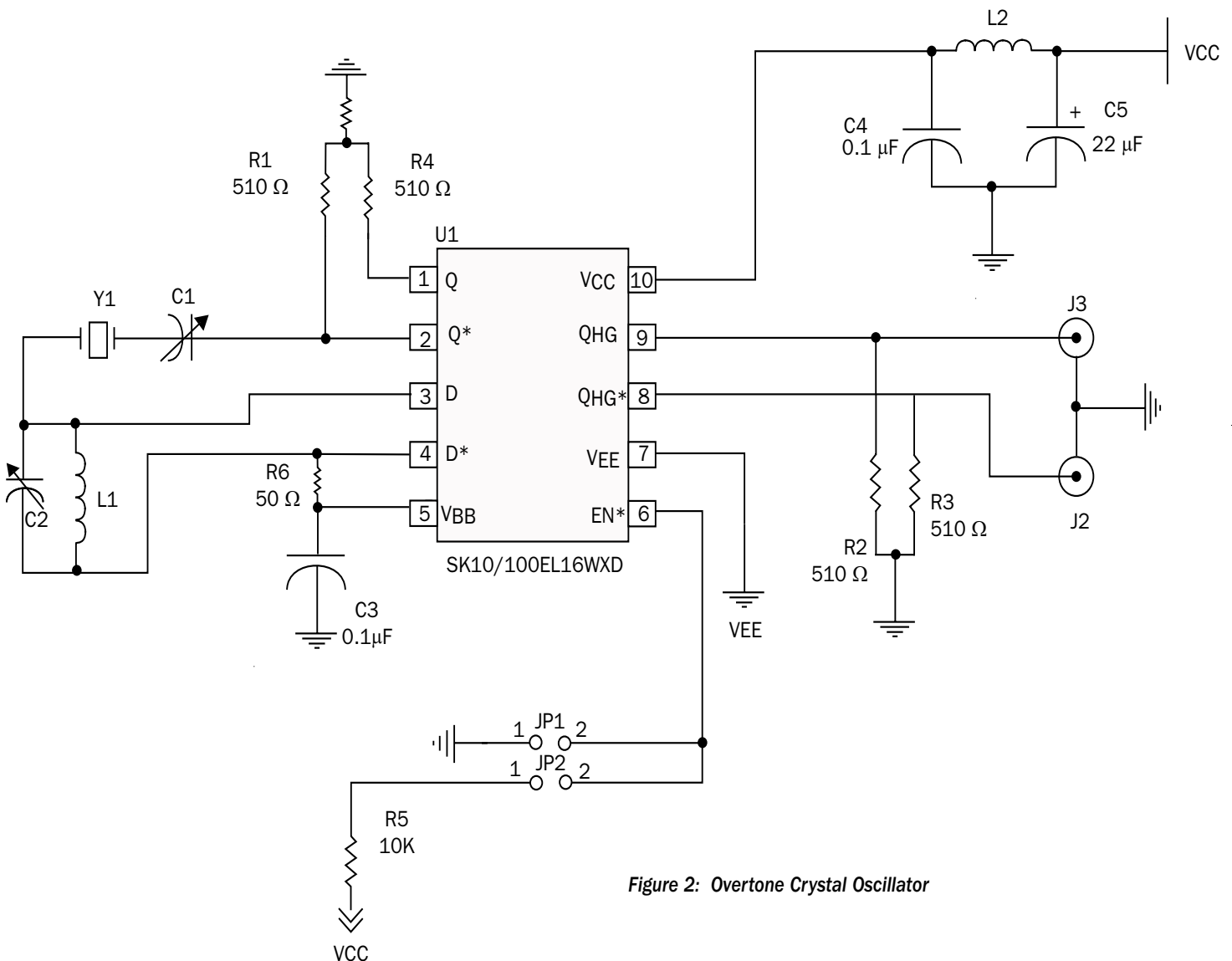


Figure 2: Overtone Crystal Oscillator

HIGH-PERFORMANCE PRODUCTS
Voltage Controlled Crystal Oscillator

A voltage-variable capacitance tuning diode is placed in series with the crystal feedback path. Changing the voltage on V_R varies the tuning diode capacitance and tunes the oscillator. The 510 K Ω resistor, R5, establishes a reference voltage for V_R and the 100 K Ω resistor, R6, isolates the tuning voltage from the feedback loop and a 0.1 μ F capacitor, C5, provides AC coupling to the tuning diode. The center frequency is set with a trimmer capacitor, C1. Deviation on either side of center is a function of the crystal frequency.

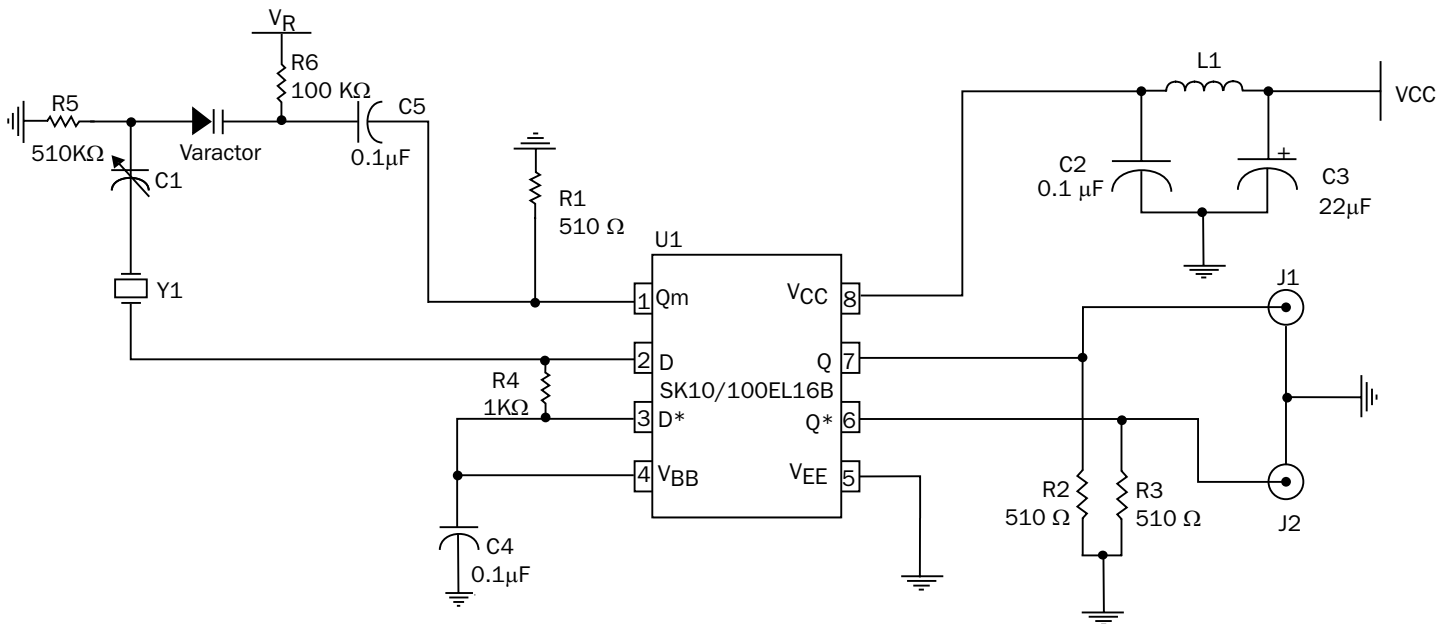


Figure 3: Voltage Controlled Crystal Oscillator

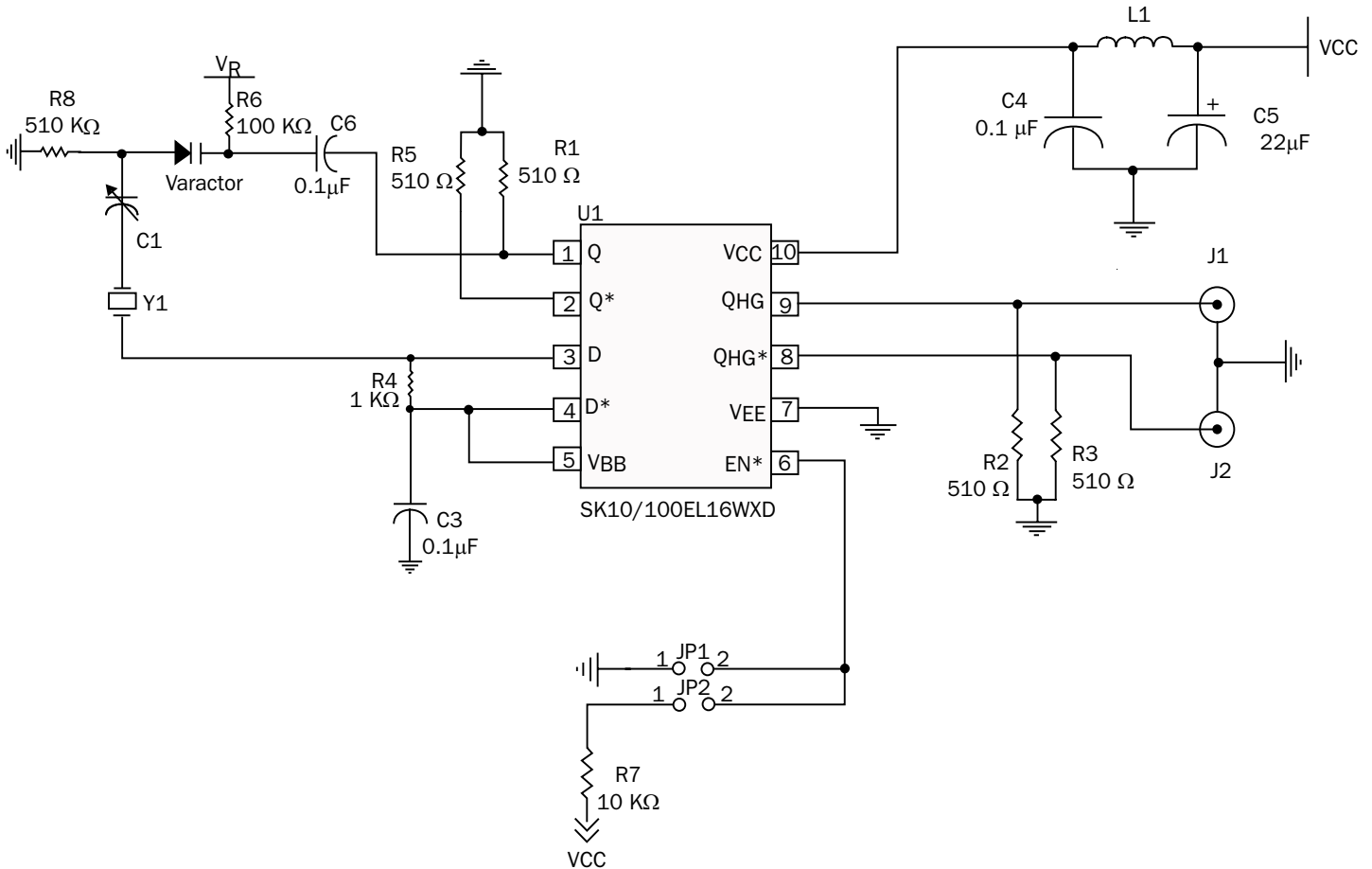
HIGH-PERFORMANCE PRODUCTS
Voltage Controlled Crystal Oscillator (con'd)


Figure 4: Voltage Controlled Crystal Oscillator

Contact Information

Division Headquarters
 10021 Willow Creek Road
 San Diego, CA 92131
 Phone: (858) 695-1808
 FAX: (858) 695-2633

Semtech Corporation
High-Performance Products Division

Marketing Group
 1111 Comstock Street
 Santa Clara, CA 95054
 Phone: (408) 566-8776
 FAX: (408) 727-8994